

EES216: Circuit Analysis

Quiz 2 — Mock Exam

curated by The Peanuts

Name..... ID..... Section..... Seat No.....

Conditions: Semi-Closed Book

Directions:

1. This exam has 6 pages (including this page).
2. Calculators (Casio 991 Series) are allowed.
3. Write your name clearly at the top of each page.
4. Reading the problem is optional but highly recommended.
5. You may bring one A3 sheet of note, which will magically become illegible the moment the exam begins.
6. Tears shed on your answer sheet may cause short circuits. Please cry responsibly.

For solution, click [here](#).


Problem 1.1

If $v(t) = 8 \cos(4t + 20^\circ) + 5 \sin(4t - 45^\circ) = A \cos(4t + \theta)$. Find A and θ by using phasor diagram:

$$A = \text{_____}, \theta = \text{_____}$$

Problem 1.2

Calculate the rms value of the waveform shown below.

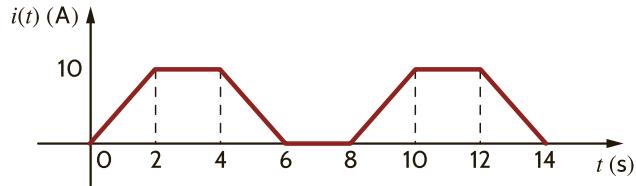


Problem 1.3

If that current (from 1.2) flows through a 10Ω resistor, find the average power absorbed by the resistor.


Problem 1.4

For the circuit shown below, determine the load impedance \mathbf{Z}_L for maximum power transfer (to \mathbf{Z}_L). Calculate the maximum power absorbed by the load (P_{\max}).

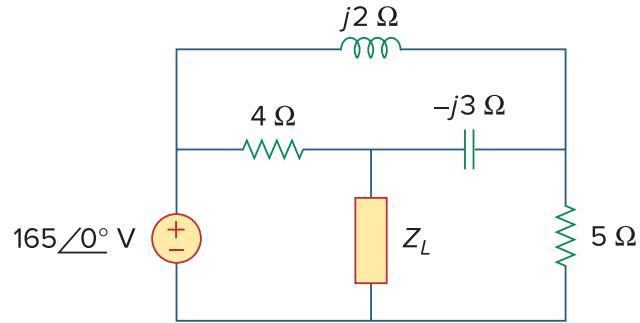

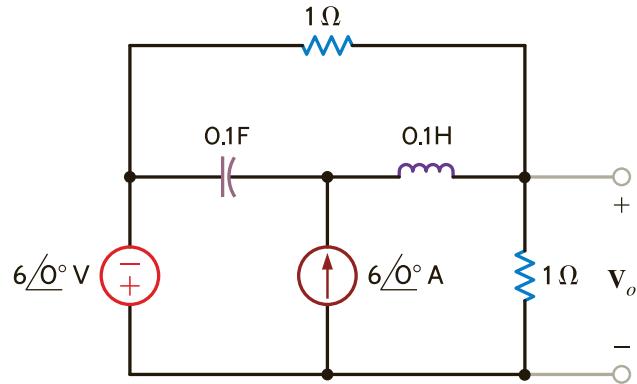Problem 2

Use **superposition** to determine \mathbf{V}_o in the circuit. The frequency is $\frac{5}{\pi}$ Hz.



Calculate the average power absorbed by each of the circuit elements.

$P_{\text{Voltage Source}} = \text{_____}$, $P_{\text{Current Source}} = \text{_____}$,

$P_{\text{Capacitor (0.1F)}} = \text{_____}$, $P_{\text{Inductor (0.1H)}} = \text{_____}$,

$P_{\text{Resistor (1Ω, top)}} = \text{_____}$, $P_{\text{Resistor (1Ω, right)}} = \text{_____}$

Problem 3

The switch in the circuit has been close for a long time and is opened at $t = 0$. For the following circuit, find $i(t)$ for $t > 0$.

